

Pinout Of 8086

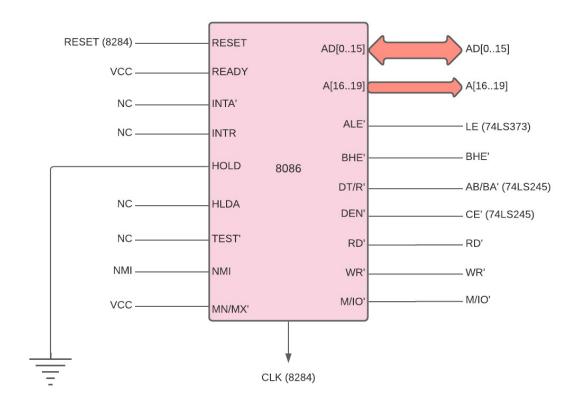


PINOUT OF 8086

Pinout Of 8086 - Data Bus Latching

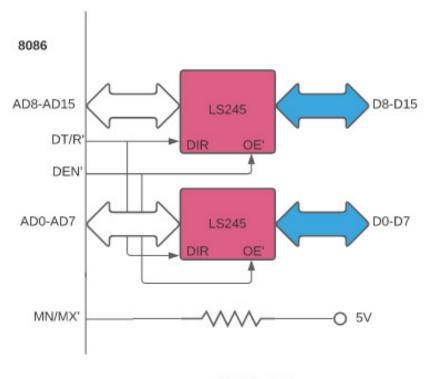


8086 Data Bus Latching


Pinout Of 8086 Address Bus

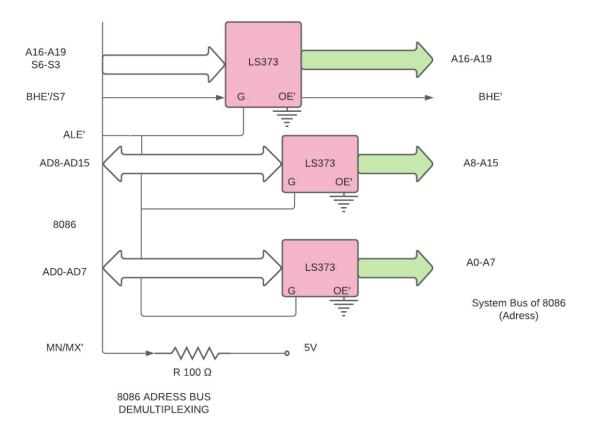


Pinout Of ROM Interfacing

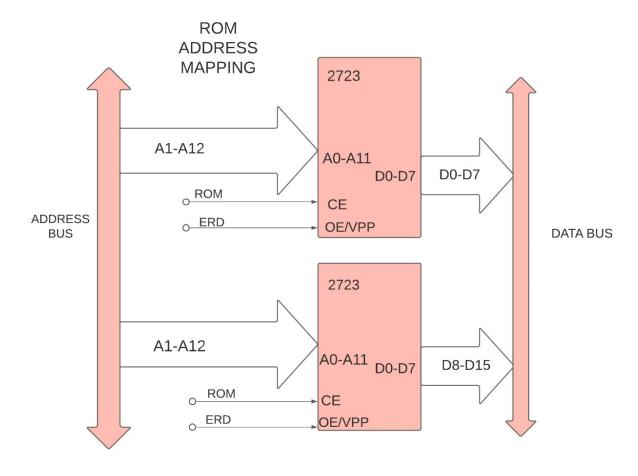

Pinout Of 8253A

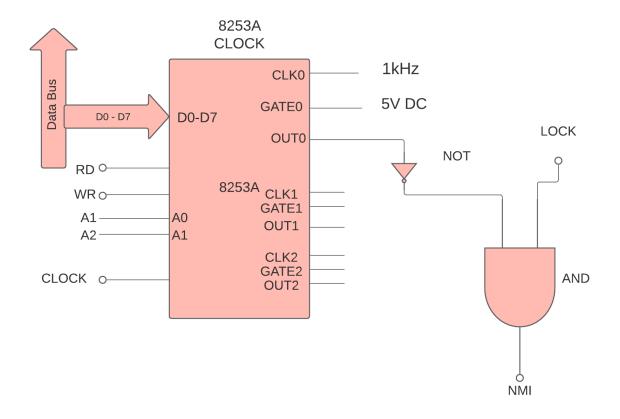



Pinout Of 8284

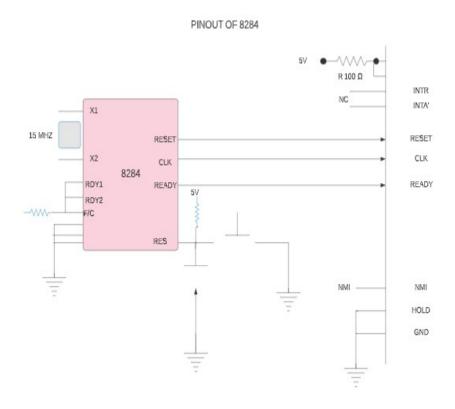

Pinout Of 8255A


PINOUT OF 8255A - 1

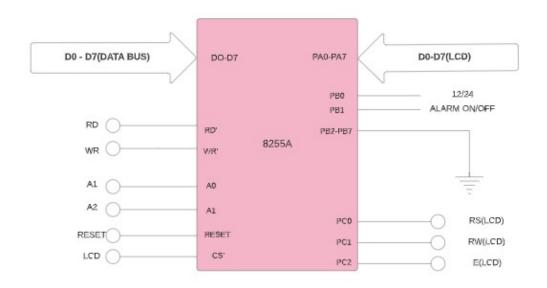

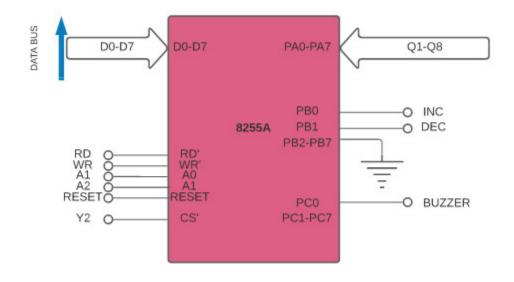


8255A #2


Pinout Of Buzzer Circuit

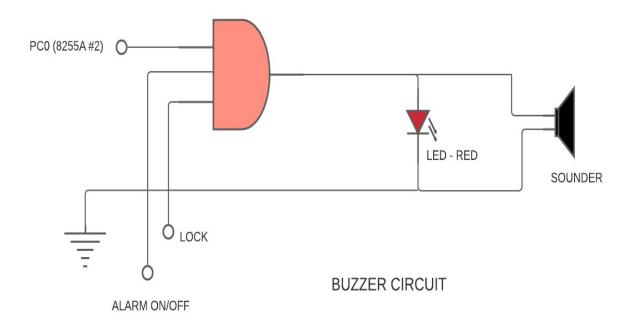

Pinout Of LCD Screen Interfacing

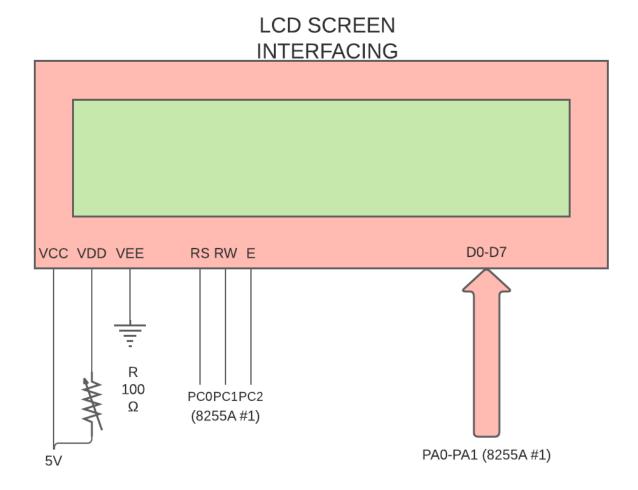


Pinout Of RAM Interfacing

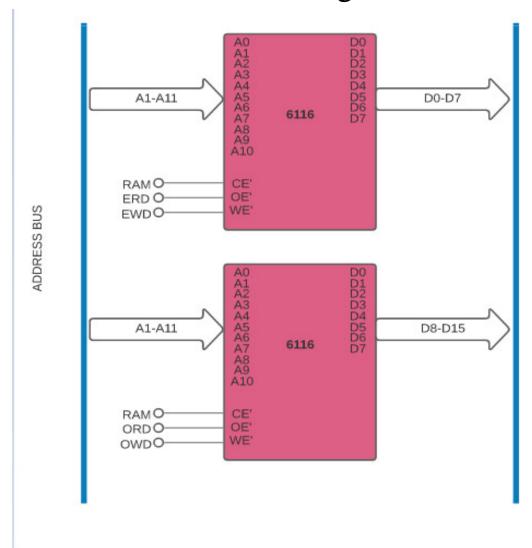


RAM INTERFACING


DATA BUS

Pinout Of I/O Mapping

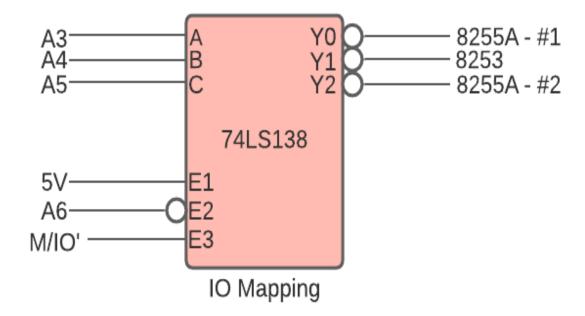


Pinout of RAM / ROM Selection

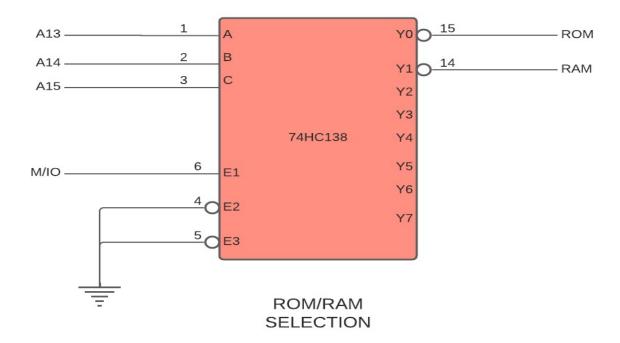

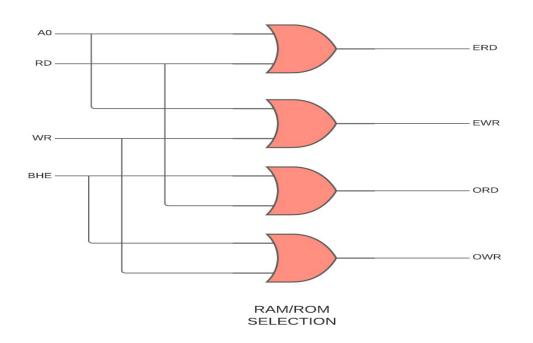


Pinout of Switches

Switches

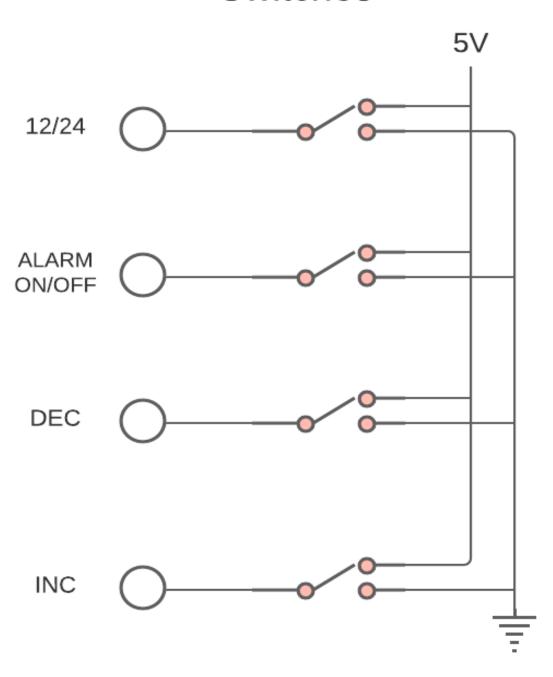

Pinout of Thumbswitch Decoder

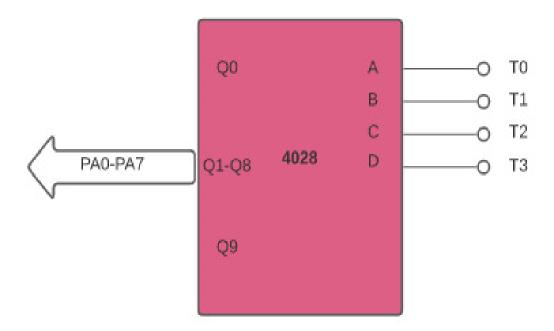

Pinout of Thumbswitch

